



# An Optical Parallel Adder Towards Light Speed Data Processing

Tohru ISHIHARA<sup>†</sup>, Akihiko SHINYA<sup>‡</sup>, Koji INOUE<sup>§</sup>,  
Kengo NOZAKI<sup>‡</sup> and Masaya NOTOMI<sup>‡</sup>

<sup>†</sup>Kyoto University

<sup>‡</sup>NTT Nanophotonics Center / NTT Basic Research Laboratories

<sup>§</sup>Kyushu University

# History of Optical Computing


## ■ Opt. computers

Intensively studied in 1970's, but CMOS computers are much more superior to the optical computers

Based on optical filters


Shadowgram

Tanida, Ichioka,  
JOSA 73, 800 (1983)

 

Hard to miniaturize

Based on optical transistors

 

SEED  
(Bell Labs.)

Miller et al.  
OQE 22, S61 (1990)


Lower performance than CMOS

## ■ Opt. interconnect

In 2000's, optical interconnects got into computers  
Intel, IBM, PETRA lead investigation (Si photonics)

Electronics → computation

Optics → communication

 

Only for interconnect ?

# Beyond Optical Communication

Chip-to-chip  
interconnect




DRAM

CPU/GPU


Intra-rack optical  
interconnect



Inter-rack optical  
interconnect

 

Network-on-Chip

 

Our focus in this talk

Optical  
Interface




RAM

Optical data-path

Functional Unit

Functional Unit


# Photonic Crystal Optical Pass Gate

   


# Why Optical PG for Data Path?

- Good at data path operation
  - ✓ Light speed operation


CMOS Delay

 

 Good at serial connection  
(light speed)




 NOT good at cascade connection  
(OE & switching delay involved)




- ✓ Good at pass/cross propagations (XOR and MUX)

XOR

 


MUX

 
 
# Optical Parallel Adder Example


- Computation can be done by just passing the optical signal through the “pass gates”




# Arithmetic Operation with OPG

- XOR/MUX-dominant data-path operation
  - ✓ Parallel Adder, Multiplier, and Barrel Shifter etc.


Full Adder (AOI logic)

 

Full Adder (modified)

 

Full Adder (OPG logic)

 


- ✓ Parallel adder as a first step
  - Can be constructed with serial connections only


# Optical Full Adder

Library Cells in  
OptiSPICE simulator  
(Optoelectronic  
circuit simulator)


Full Adder (AOI logic)

 

Full Adder (OPG logic)

 


1: through  
0: cross

 

Phase shifter




OE conversion

 

Y splitter






X coupler

 




# Design and Evaluation: 16-bit Adder

   


 
# OptiSPICE Simulation Results

- Optoelectronic Circuit Simulator (HSPICE engine)
- Light-speed parallel adder operation confirmed
  - Per digit delay: ~1ps, Initial OE and switching delay: ~25ps



  
# 16-bit CMOS Adder as Comparison

16 nm High Performance CMOS Technology PTM



 
# Comparison

- 16-bit parallel adder is designed with OPG
- Light-speed operation is confirmed
  - Per digit delay: OPG ~1 ps, CMOS 22 ps
  - 16-bit total delay: OPG ~40 ps, CMOS 350 ps



 
# Wavelength Division Multiplexing

- Exploit WDM for reducing the circuit size
- $\lambda_1$  represents carry,  $\lambda_2$  represents carry bar


 
# OptiSPICE Simulation Results

- Different wavelengths for **carry** and **carry bar**
  - This structure reduces RC delay in electric control signal
  - Per digit delay:  $\sim 1\text{ps}$ , Initial OE and switching delay:  $\sim 25\text{ps}$



# Related Work

- Parallel adder based on shared BDD

T. Asai, Y. Amemiya, and M. Kosiba, "A Photonic-Crystal Logic Circuit Based on the Binary Decision Diagram," in *Proc. of IWPECS*, T4-14, March 2000.


72% loss per digit

Max fan-out = 4

Large power loss

Serial connections  
= # digits x 2

Large power loss

 

# Summary

- 16-bit parallel adder is designed with OPG
- Light-speed WDM operation confirmed
  - Per digit delay: OPG ~1 ps, CMOS 22 ps
  - 16-bit total delay: OPG ~40 ps, CMOS 350 ps
- Power loss is an issue to be resolved
  - Per digit power loss ~20%
- Future work
  - Extend this to more complicated functions




# Acknowledgement

This work is partly supported by **CREST** (Core Research for Evolutional science and Technology) of **JST** (Japan Science and Technology Corporation)

# Backup
 
# Results of OptiSPICE Simulation

- Optoelectronic Circuit Simulator (HSPICE engine)
- Light-speed parallel adder operation confirmed
  - Per digit delay: ~1ps, Initial OE and switching delay: ~10ps
  - 8-bit CMOS adder with 16nm HP PTM: 174 ps



# Power Loss in Adder Operation

Power halves every 2 digits

